
Organización de Computadoras – Fac. de Informática – Prof. Jorge Runco Curso 2015 - Práctica 4 – Lógica y Compuertas

6)

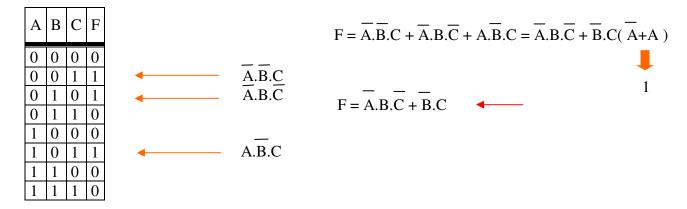

7) Segmento f

A	В	С	D	Decimal	f
0	0	0	0	0	1
0	0	0	1	1	0
0	0	1	0	2	0
0	0	1	0	3 4	0
0	1	0	1	5	1
0	1	1	0	6	1
0	1	1	1	7	0
1	0	0	0	8	1
1	0	0	1	9	1
1	0	1	0	-	0
1	0	1	0	-	0
1	1	0	1		0
1	1	1	0	_	0
1	1	1	1	-	0